

## Magdy's Assignment (1) FPGA Design

### Question (1): -

Using only logic gates, design a 2-bit full adder with carry. Here is a partial truth table for the circuit.

INPUTS					OUTPUTS		
A0	A1	B0	B1	Ci	S0	S1	Co
0	0	0	0	0	0	0	0
1	0	0	0	0	1	0	0
0	1	0	0	0	0	1	0
1	0	1	0	0	0	1	0
0	1	0	1	0	0	0	1
0	1	0	0	1	1	1	0
1	0	1	0	1	1	1	0
1	1	1	1	1	1	1	1

Where A and B are inputs, Ci is Carry in, Si is output, and Co is Carry out.

Draw a schematic showing the gate interconnections. Include either a Boolean equation or an explanation of your design that matches the schematic you submit.

### Solution


#### 1<sup>st</sup> Solution:

**Explanation:** Using 4 XORs, 4 AND gates, 2 OR gates.

$$S_0 = A_0 \text{ XOR } B_0 \text{ XOR } C_{in}$$

$$S_1 = A_1 \text{ XOR } B_1 \text{ XOR } C_{0out}, \text{ where } C_{0out} = (A_0 \text{ AND } B_0) \text{ OR } (C_{in} \text{ AND } (A_0 \text{ XOR } B_0))$$
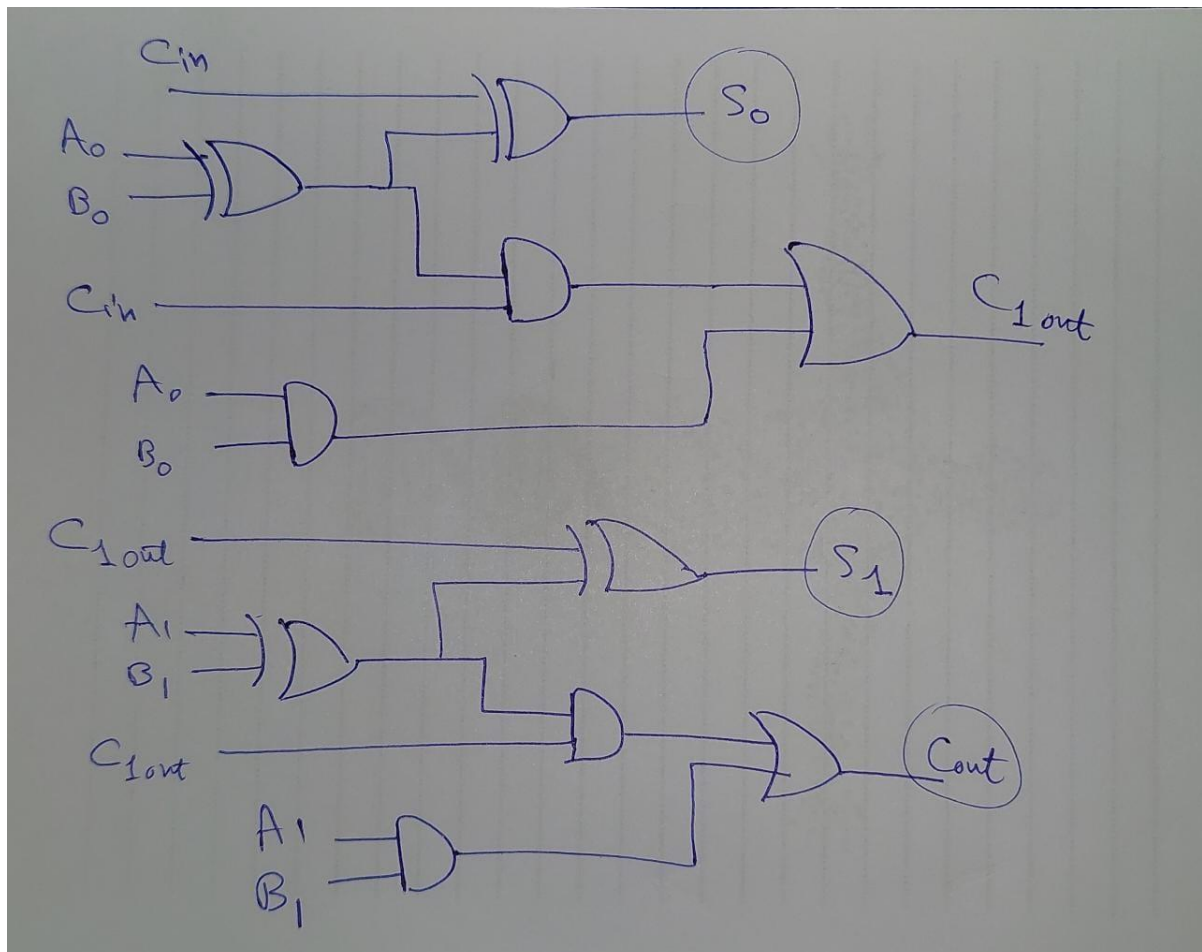
$$C_0 = (A_1 \text{ AND } B_1) \text{ OR } (C_{0out} \text{ AND } (A_1 \text{ XOR } B_1))$$




## 2nd Solution:

**Explanation:** Using 5 Inputs and their inverters, 11 AND gates, 3 OR gates.

$$S_0 = A_0 \bar{A}_1 \bar{B}_0 \bar{B}_1 \bar{C}_i + \bar{A}_0 A_1 \bar{B}_0 \bar{B}_1 C_i + A_0 \bar{A}_1 B_0 \bar{B}_1 C_i + A_0 A_1 B_0 B_1 C_i$$

$$S_1 = \bar{A}_0 A_1 \bar{B}_0 \bar{B}_1 \bar{C}_i + A_0 \bar{A}_1 B_0 \bar{B}_1 \bar{C}_i + \bar{A}_0 A_1 \bar{B}_0 B_1 C_i + A_0 \bar{A}_1 B_0 B_1 C_i + A_0 A_1 B_0 B_1 C_i$$
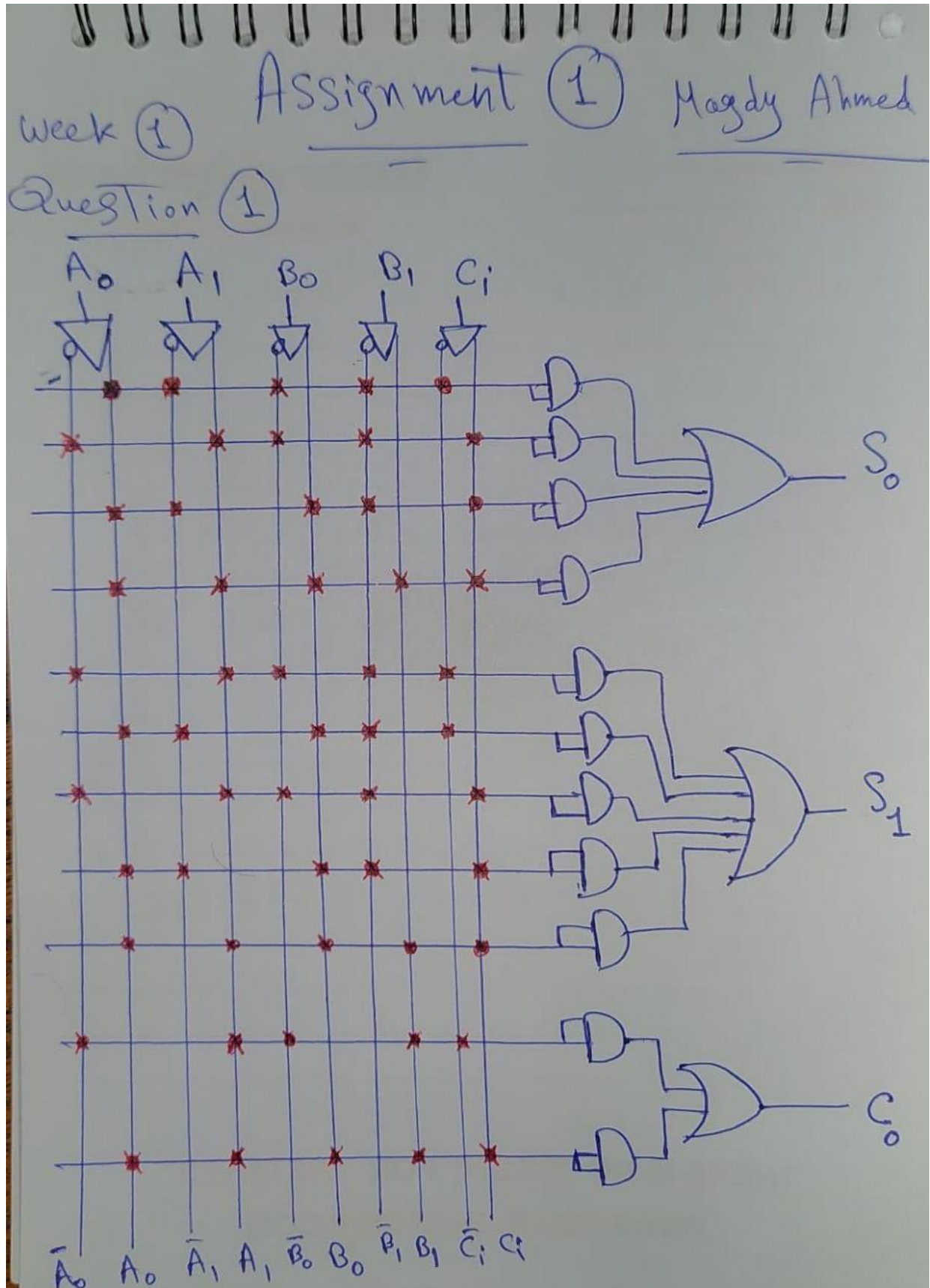
$$C_o = \bar{A}_0 A_1 \bar{B}_0 B_1 \bar{C}_i + A_0 A_1 B_0 B_1 C_i$$




## Question (2): -

Show how the logic equation  $(A \text{ AND NOT}(B)) \text{ OR } (C \text{ AND NOT}(D))$  can be implemented using the following:

### Solution

A. The PLA shown here:

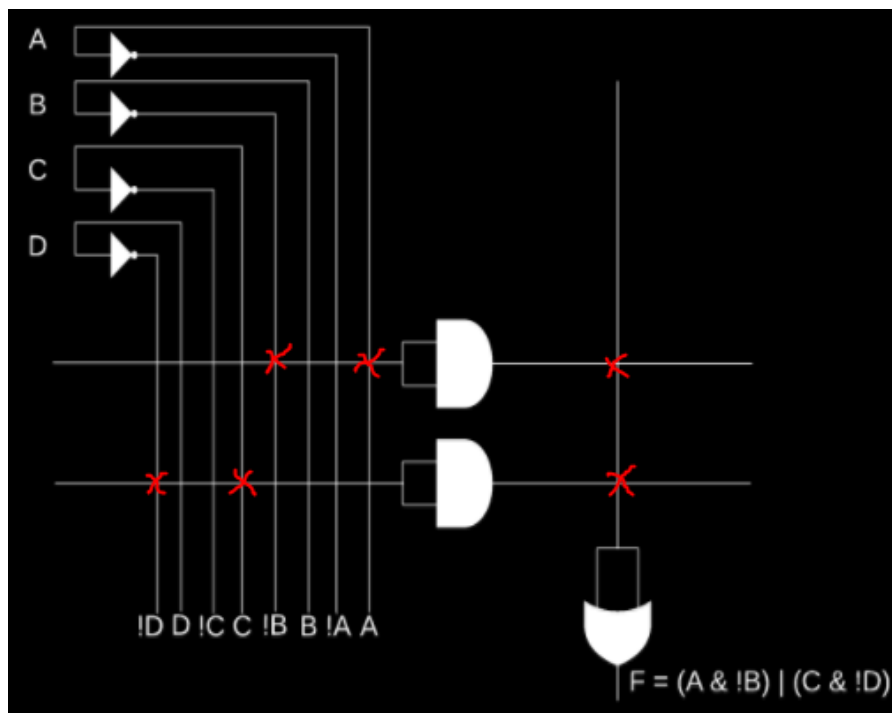

**Explanation:** Fuse the wires of  $(A, !B)$  for the first AND gate  $(C, !D)$  for the Second AND then make ORing

B. The LUT shown here:

RAM CONTENTS				
Address				Output Data
A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

**Explanation:** Apply  $F = (A \& !B) | (C \& !D)$  to each combination of inputs the put it in the Truth Table.